


* Lecture 4 *

Electronics

Low pass filter:


- it is a filter that passes signals with a frequency lower than a certain value. «Cut off value»
- هو مرشح يقوم بتمرير الإشارات ذات الترددات المنخفضة ويقوم بتقليل شدة الإشارات ذات الترددات الأعلى منه تردد الإيقاف.

$$* f_c = \frac{1}{\pi R C}$$

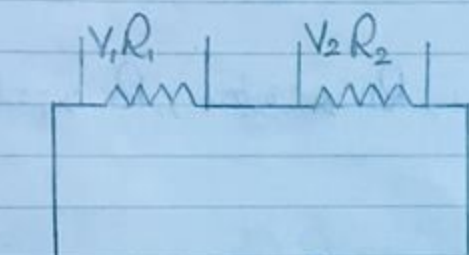


$$\text{If : } R_2 \gg R_1 \\ \therefore V_2 \gg V_1$$

Low pass
Low frequencies


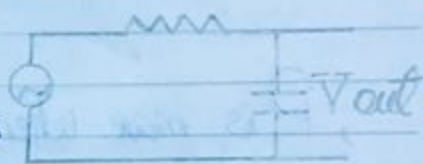


High pass
High frequencies

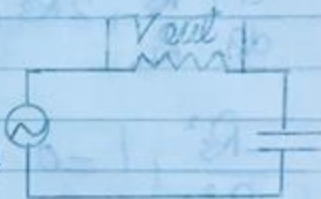

* Design high pass filter and low pass filter.

* L-C Circuits *

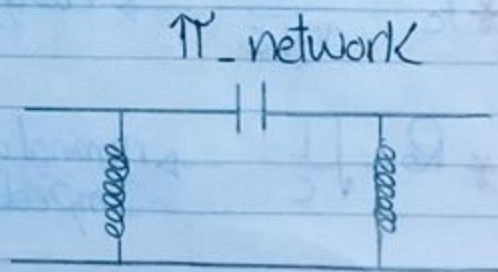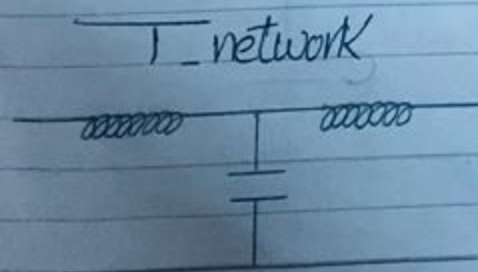


- each of them is used in Low, High filters.

* Prove that M.P.T takes place when the resistance of the Load is equal to the resistance of the Source.

R_s : internal resistance

R_L : Load resistance

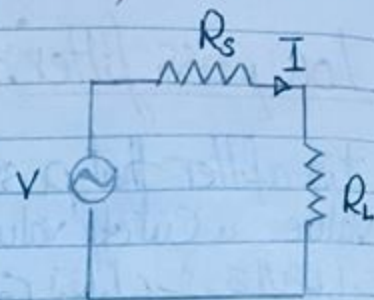

Proof: $I = \frac{V}{R_s + R_L}$, $P = IV = I^2 R_L$

$$\therefore P = \left(\frac{V^2}{R_s^2 + 2R_s R_L + R_L^2} \right) R_L = \frac{V^2}{\frac{R_s^2 + 2R_s R_L + R_L^2}{R_L}} = \frac{V^2}{\frac{R_s^2}{R_L} + 2R_s + R_L}$$

, P is max. when $\left(\frac{R_s^2}{R_L} + 2R_s + R_L \right)$ is min. , $R_L \rightarrow$ متغيرة , $R_s \rightarrow$ ثابتة


$$\therefore \frac{d}{dR_L} \left(\frac{R_s^2}{R_L} + 2R_s + R_L \right) = \frac{-R_s^2}{R_L^2} + 1$$

$$\frac{-R_s^2}{R_L^2} + 1 = 0 \quad , \therefore R_s^2 = R_L^2 \quad , \therefore \boxed{R_s = R_L} \text{ matching case}$$

Low pass filter in L-C Circuits:-

* $f_c = \frac{1}{\pi \sqrt{LC}}$ \rightarrow Cut off frequency

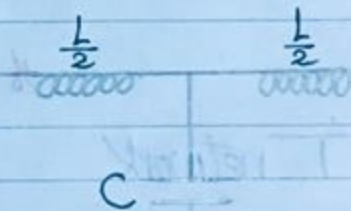* $R_0 = \sqrt{\frac{L}{C}}$ \rightarrow nominal "characteristic" Impedance مقاومة الفلتر




* Determine the cut off frequency and nominal impedance for low pass T-Connected Circuit.

$$\rightarrow f_c = \frac{1}{\pi \sqrt{LC}}, \quad \frac{1}{2} = 100 \text{ mH}, \quad \therefore L = 200 \text{ mH}$$

$$f_c = \frac{1}{\pi \sqrt{200 \times 10^{-3} \times 0.2 \times 10^{-6}}} = 1.6 \text{ kHz}$$

$$R = \sqrt{\frac{L}{C}} = \sqrt{\frac{200 \times 10^{-3}}{0.2 \times 10^{-6}}} = 1000 \Omega = 1 \text{ k}\Omega$$

- Convert T-network to π network:

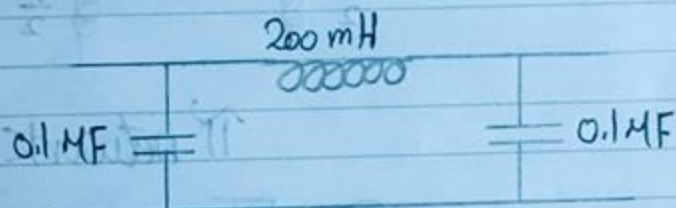


- الشرط الذي يلزم توافقه في الدائرة لتعمل كفلتر بانج هو شرط التكافؤ matching Condition

* Prove that: $L = \frac{R_0}{\pi f_c}$, $C = \frac{1}{\pi R_0 f_c}$


* A filter circuit of nominal impedance 600Ω and its cut off frequency = 5 MHz. Design low pass filter in T, π Configuration.

$$\rightarrow L = \frac{R_0}{\pi f_c} = \frac{600}{\pi \times 5 \times 10^6} = 3.8 \times 10^{-5} \text{ H} = 38 \mu\text{H}$$
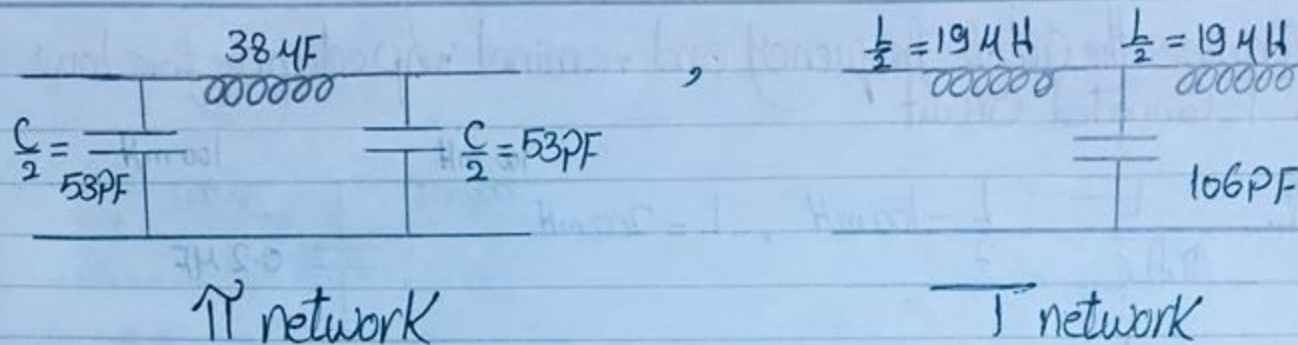
$$C = \frac{1}{\pi R_0 f_c} = \frac{1}{\pi \times 600 \times 5 \times 10^6} = 1.06 \times 10^{-10} \text{ F} \times 10^{12} = 106 \text{ pF}$$



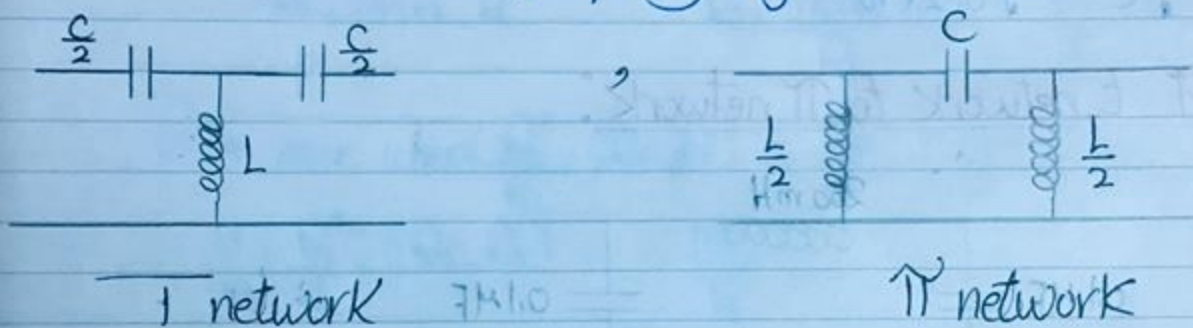2) High pass filter: it is a filter that passes signals with a frequency higher than a certain value.



$$* f_c = \frac{1}{4\pi\sqrt{LC}}$$

$$* R_0 = \sqrt{\frac{L}{C}}$$

$$* L = \frac{R_0}{4\pi f_c}$$

$$* C = \frac{1}{4\pi R_0 f_c}$$

* Sheet: Determine a filter network passes a single wavelength "frequency" تمرکز تردد، امواج