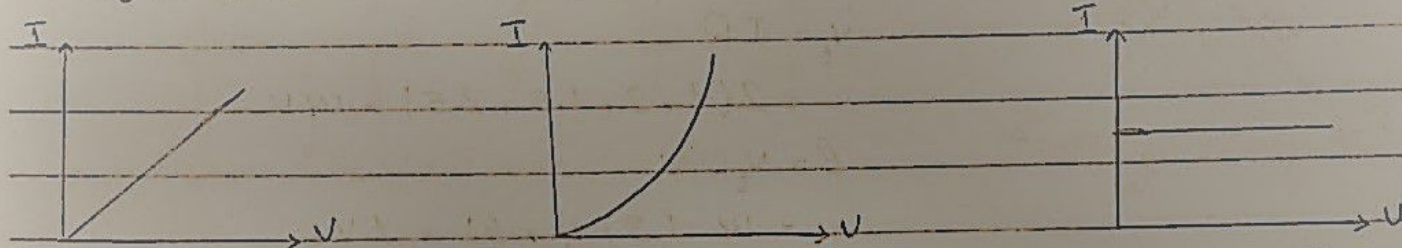


"lecture 1"

→ Circuit Components:

→ Superconductors → $0 = \frac{1}{\rho} \frac{dV}{dI}$



"linear Component"

"non linear Component"

"D.C"

Ohm → $V = IR$

" $I \propto \frac{1}{R}$ "


→ Capacitor:

→ Why metals are good conduction?

Because they are rich with free electrons.

1) Energy Storage system → $X_C = \frac{1}{2\pi f C}$

2) By Pass →

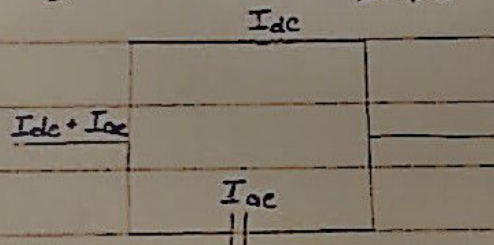

→ Charging → accumulation of charge carriers.

$$V = V_0 e^{-\frac{t}{R_c}}$$

→ C = Capacity / R = Resistance / R_c = Time Constant / V_0 = "V" at "t=0".

→ $R_c = t$

$$V = V_0 e^{-\frac{t}{R_c}} = \frac{V_0}{e}$$



→ D.C circuit Theories:

1) Kirchhoff's laws:

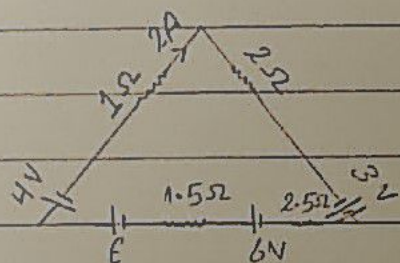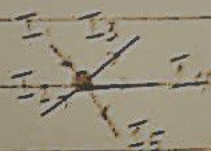a) At any junction in an electric circuit the total current flowing toward that junction must equal to the total current flowing away from that junction.

" $\sum I = 0$ " → "Current law"

$$\rightarrow I_1 + I_2 - I_3 - I_4 - I_5 = 0$$




$$V_t = I R$$

$$= 2(1 + 2 + 1.5 + 2.5) = 14V$$

$$P = \sum V_t$$

$$= 14 - (3 + 4 + 6) = 1V$$

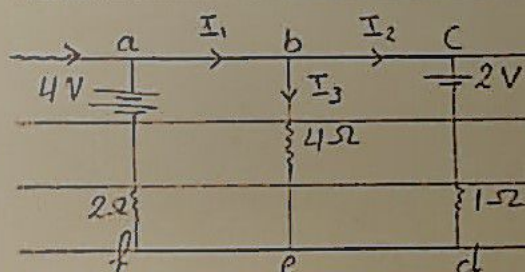b) In any closed loop in a network the algebraic sum of the voltage drops taken around the loop is equal to the resultant emf acting in that loop. " $\sum V_B = \sum I R$ ", "Voltage law"



1) loop abch:

$$4 = 4I_3 + 2I_1 \rightarrow (1)$$

2) loop bcde:

$$2 = I_2 - 4I_3 \rightarrow (2)$$

3) by using current law:

$$\sum I = 0$$

$$\therefore I_1 - I_2 - I_3 = 0 \rightarrow (3)$$

$$I_1 = I_2 + I_3$$

$$4 = 4I_3 + 2(I_2 + I_3) \rightarrow 4 = 6I_3 + 2I_2$$

$$2 = I_2 - 4I_3 \quad (\times 2)$$

$$4 = 2I_2 + 6I_3$$

$$14I_3 = 0 \rightarrow I_3 = 0$$

$$I_2 = 2A \quad \& \quad I_1 = 0 + 2 = 2A$$