

* Lecture 3 *

* R-L-C Circuits :-

$$Z = \sqrt{R^2 + (X_L - X_C)^2}, \quad \tan \phi = \frac{X_L - X_C}{R} \quad \text{or} \quad \frac{X_C - X_L}{R}$$

- Very Important :-

→ The following 3 impedances are connected in series across 40V, 20 KHz:

1. Resistance of 8 ohm
2. Coil of Inductance $L = 130 \text{ mH}$, $R = 5 \text{ } \Omega$
3. Resistance = $10 \text{ } \Omega$, $C = 0.25 \text{ } \mu\text{F}$

- Calculate :-

1. The Circuit Current " I "
2. Phase Shift " ϕ "
3. The Voltage load across each impedance.



$$\begin{aligned} X_L &= 2\pi FL \\ &= 2\pi \times 20 \times 10^3 \times 130 \times 10^{-6} = 16.34 \text{ } \Omega \\ X_C &= \frac{1}{2\pi FC} = \frac{1}{2\pi \times 20 \times 10^3 \times 0.25 \times 10^{-6}} \\ &= 31.8 \text{ } \Omega \end{aligned}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{23^2 + (31.8 - 16.34)^2} = 27.7 \text{ } \Omega$$

$$I = \frac{V}{Z} = \frac{40}{27.7} = 1.44 \text{ A} \rightarrow (1)$$

$$\begin{aligned} \tan \phi &= \frac{X_C - X_L}{R} = \frac{31.8 - 16.34}{23} \\ &= 0.67 \end{aligned}$$
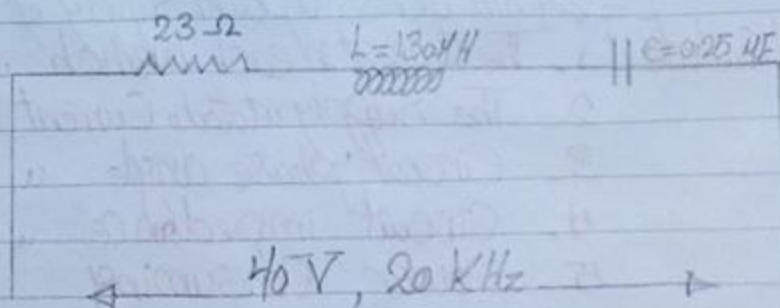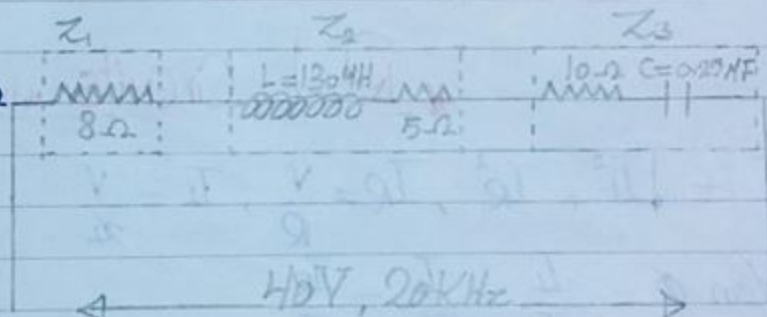
$$\therefore \phi = 33.9^\circ \rightarrow (2)$$



$$Z_1 = 8 \Omega, Z_2 = \sqrt{X_L^2 + R^2} = \sqrt{(16.34)^2 + 5^2} = 17 \Omega$$

$$Z_3 = \sqrt{X_C^2 + R^2} = \sqrt{(31.8)^2 + 10^2} = 33.34 \Omega$$

* Resonance Case *

حالة الرنين

Conditions:- $V_L = V_C$, $Z = R$, $I = \frac{V}{R}$, $X_L = X_C$


$$f = \frac{1}{2\pi\sqrt{LC}} \rightarrow \text{resonance frequency} \quad \text{تردد الرنين}$$

Resonance frequency doesn't depend on R and it depends only on L, C .
 لا يعتمد تردد الرنين على المقاومة، ولكنه يعتمد فقط على الحث الذاتي لللف و سعة المكثف.
 وتكون للدارة خصائص أومية فقط.

* R-L Circuits "in parallel" *

$$I = \sqrt{I_L^2 + I_R^2}, I_R = \frac{V}{R}, I_L = \frac{V}{X_L}$$
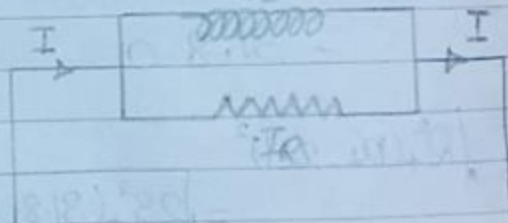
$$\tan \phi = \frac{I_L}{I_R} = \frac{I_L}{I} = \frac{I_R}{I}$$



Problem:- A 20Ω resistor is connected in parallel with inductance $L = 2.4 \text{ mH}$ across a power supply of 60 V , 1 kHz

- Calculate:
1. The Current in each branch. " I_L, I_R "
 2. The Supply "total" Current " I "
 3. Circuit phase angle " ϕ "
 4. Circuit impedance " Z "
 5. power Consuming

$$\rightarrow X_L = 2\pi fL = 2\pi \times 1 \times 1000 \times 2.4 \times 10^{-3} = 15.08 \Omega$$

$$, I_L = \frac{V}{X_L} = \frac{60}{15.08} = 3.98 \text{ A}$$


$$, I_R = \frac{V}{R} = \frac{60}{20} = 3 \text{ A}$$

$$, I = \sqrt{I_L^2 + I_R^2} = \sqrt{(3.98)^2 + 3^2} = 4.98 \text{ A}$$

$$, \tan \phi = \frac{I_L}{I_R} = \frac{3.98}{3} = 1.33, \therefore \phi = 52.99^\circ$$

$$, Z = \frac{V}{I} = \frac{60}{4.98} = 12 \Omega$$
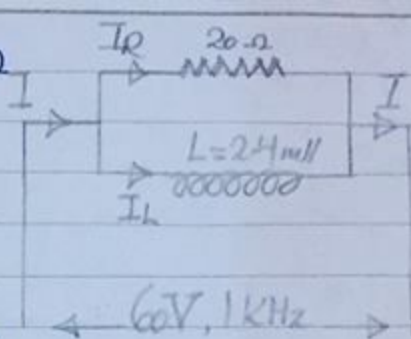
$$, P_w = I_R^2 R = 3^2 \times 20 = 180 \text{ watt}$$



* لا يورث اية حرارة في الملف
لأنه يخزن الطاقة على هيئة
مجال مغناطيسي.